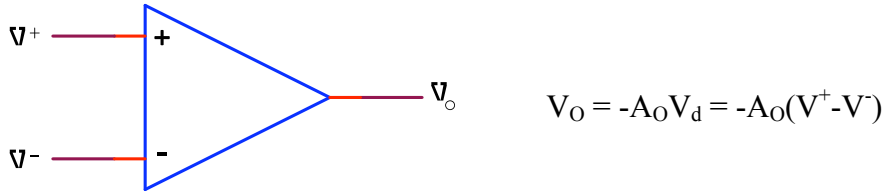



Analog Electronics Lecture 1 – Operational Amplifiers

An Ideal Operational Amplifier – Op-Amp:



V_d is the differential input voltage or the mathematical difference between the voltage at V^+ and V^- . A_O is the gain.

A real Op-Amp

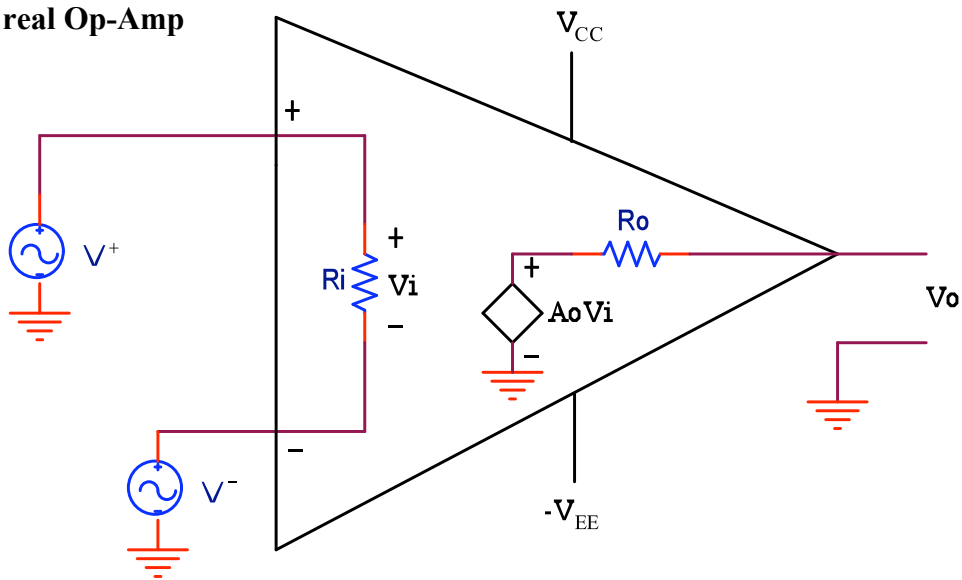

Ideally:

$$A_O \rightarrow \infty$$

$$R_i \rightarrow \infty$$


$$R_O \rightarrow 0$$

Reality:


A_O is less than ∞ and is dependant on frequency.

R_i ranges from $2M\Omega$ to $1T\Omega$ ($1 \times 10^{12}\Omega$).

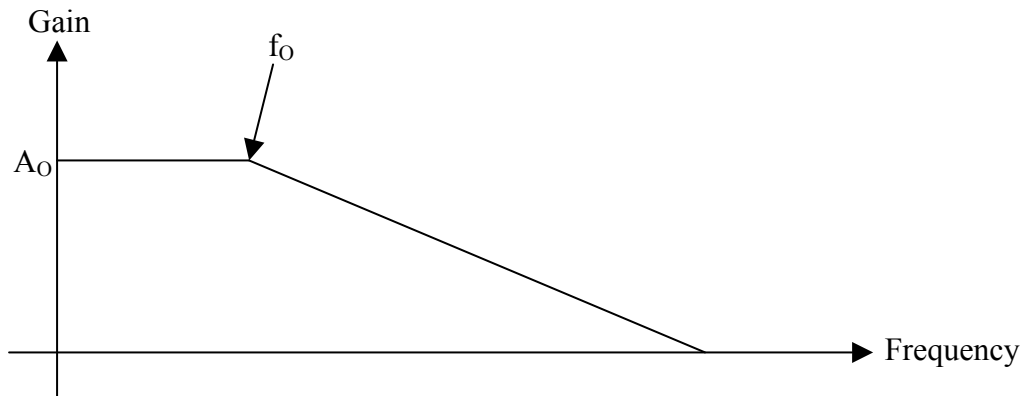R_O ranges from 10Ω to 100Ω , typically 75Ω .



Control Theory

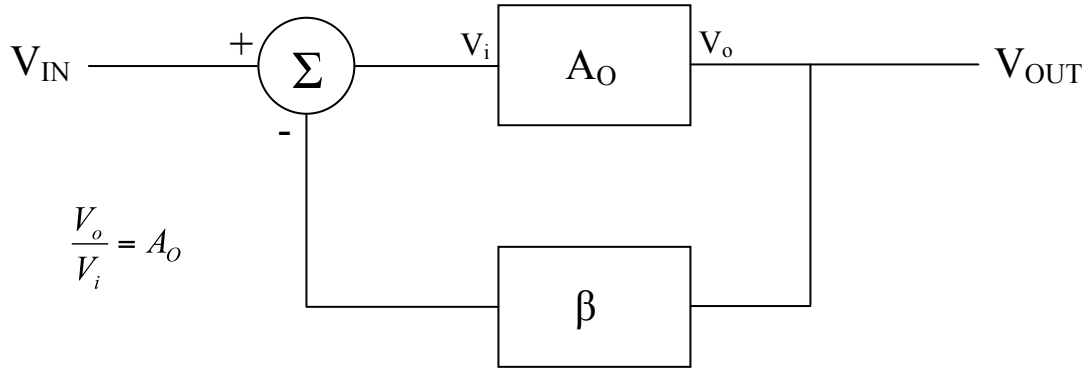


$$\frac{V_o}{V_i} = A_O$$


$$\text{System Gain} = \frac{V_{OUT}}{V_{IN}} = \frac{A_O}{1 + A_O\beta}$$

Applications of the Op-amp

- The Voltage Follower

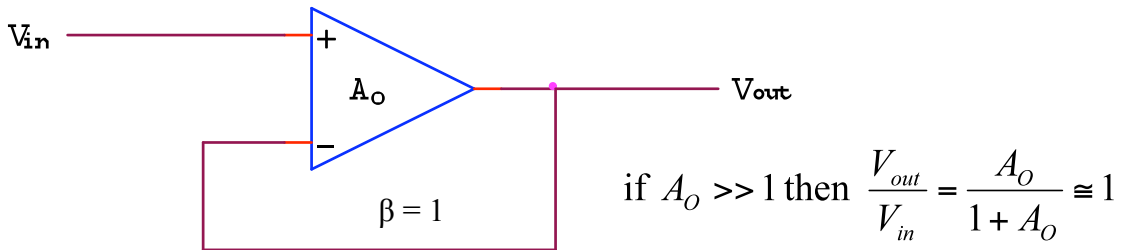


- The Non-Inverting Amplifier

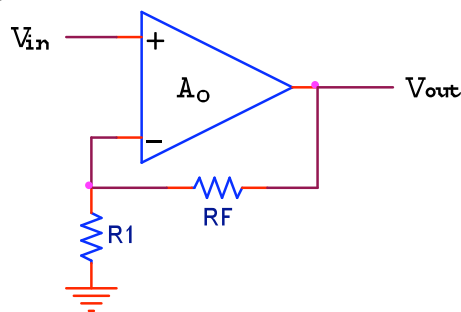


$$\text{Here } \beta = \frac{R_1}{R_1 + R_F} \text{ Therefore, } A = \frac{A_O}{1 + A_O \frac{R_1}{R_1 + R_F}} = \frac{R_1 + R_F}{\frac{1}{A_O}(R_1 + R_F) + R_1} \cong \frac{R_1 + R_F}{R_1} = \frac{1}{\beta}$$

- **The Inverting Amplifier**

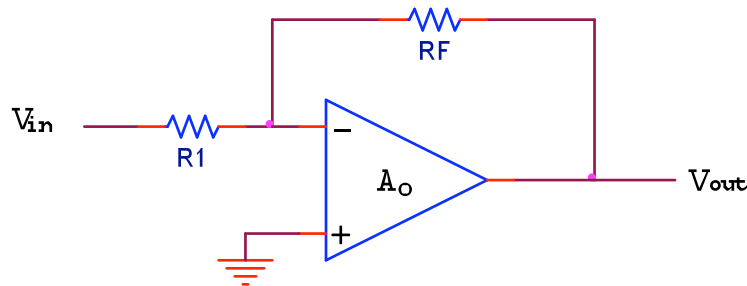


Here $\beta = -\frac{R_1}{R_F}$ Therefore, $A = \frac{A_O}{1 - A_O \frac{R_1}{R_F}} = \frac{R_F}{\frac{1}{A_O} R_F - R_1} \cong -\frac{R_F}{R_1} = \frac{1}{\beta}$

- **The Differential Amplifier**

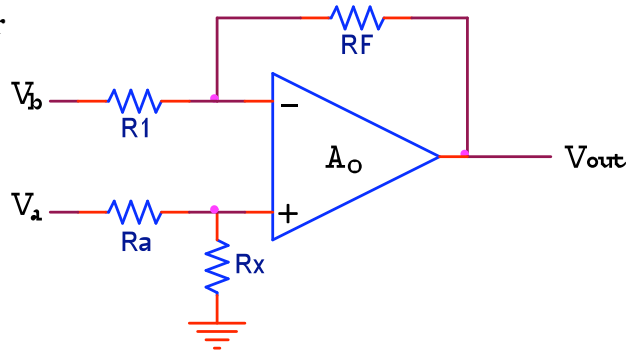


$V_{out} = -\frac{R_F}{R_1} V_b + \left(1 + \frac{R_F}{R_1}\right) \left(\frac{R_x}{R_x + R_a}\right) V_a$ if $R_a = R_1$ and $R_F = R_x$ then $V_{out} = (V_a - V_b) \frac{R_F}{R_1}$


- **The Integrator**

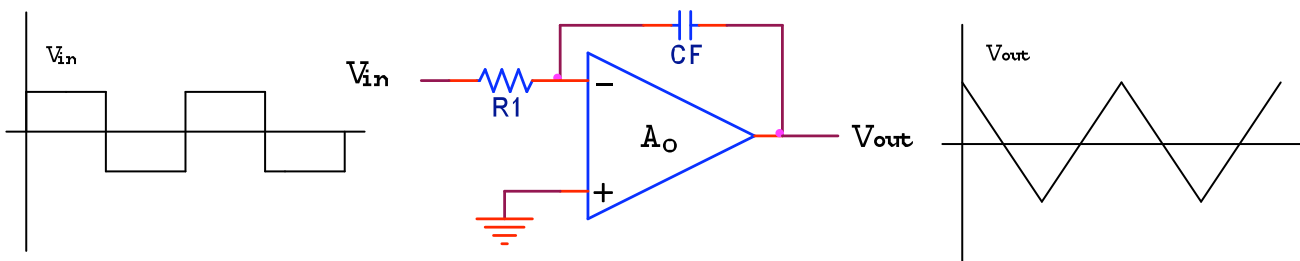

- **The Differentiator**

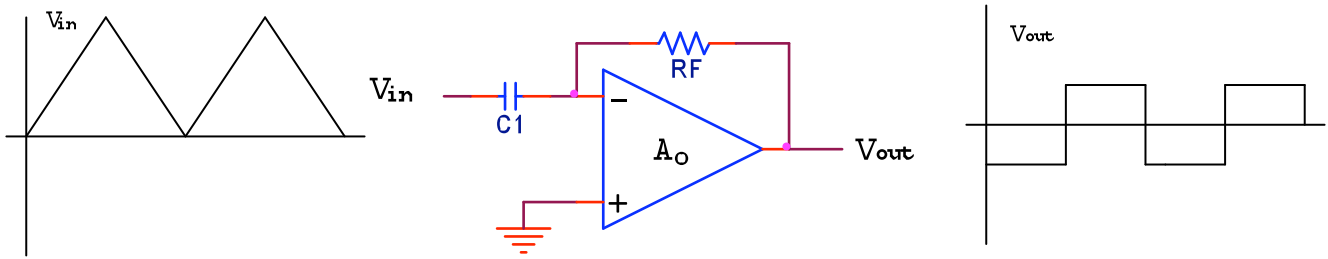

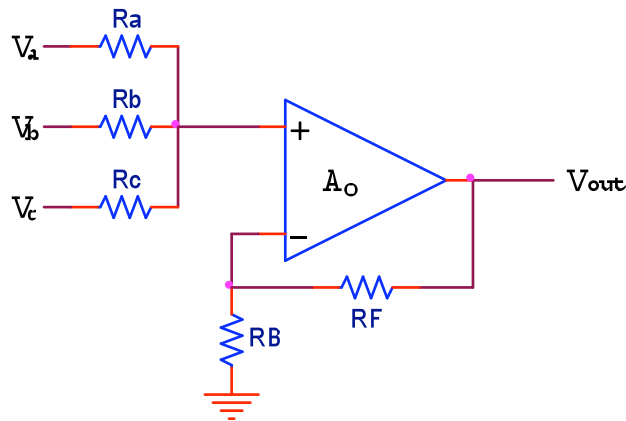- **The Non-Inverting Summing Amplifier**



$$V_{out} = \left(1 + \frac{R_F}{R_B}\right) \left(\frac{R_A}{R_a} V_a + \frac{R_A}{R_b} V_b + \frac{R_A}{R_c} V_c \right) \text{ where } R_A = \frac{1}{\frac{1}{R_a} + \frac{1}{R_b} + \frac{1}{R_c}}$$

$$\text{If } R_a = R_b = R_c \text{ then } V_{out} = \left(1 + \frac{R_F}{R_B}\right) \left(\frac{V_a + V_b + V_c}{3} \right)$$